

## 2 MARKS QUESTION

- Ans) Define Slew Rate and CMRR.
- Ans) Determine  $\beta_{dc}$  and  $I_{CBO}$  if  $I_E = 5\text{mA}$ ,  $I_C = 4.95\text{mA}$   
"  $I_{CEO} = 20\mu\text{A}$ .
- Ans) What is Modulation and Modulation Index.
- Ans) Define Ripple factor.
- Ans) Why BJT is called Current Controlled device.
- Ans) Write Ideal characteristics of op-Amp.
- Ans) Distinguish b/w avalanche and Zener breakdown.
- Ans) How MOSFET can be voltage controlled device.
- Ans) The BJT circuit has  $I_C = 10\text{mA}$  and  $\alpha = 0.98$ . Determine the value of  $\beta$  and  $I_E$ .
- Ans) Sketch the input and output characteristics of CB BJT configuration.
- Ans) Write down the stability factor for BJT amplifier.
- Ans) Minimize the Boolean expression  $(x+y)(x+y')$
- Ans) What do you mean by Leakage Current?
- Ans) Convert  $(4021.25)_{10} = ( \quad )_2$
- Ans) An OP-Amp has a differential gain of  $10^3$  and a CMRR of 100, input voltage are  $100\mu\text{V}$  and  $0.01\text{V}$ . Determine the Output Voltage.

Ques) Differentiate depletion and Enhancement type MOSFET.

Ques) Convert the  $(6089.25)_{10} \rightarrow ( )_8$

Ques) Define AM.

Ques) Draw a circuit of an Voltage follower and find an expression for its voltage gain.

Ques) Draw the characteristics of transfer characteristics of D-MOSFET.

Ques) Why E-MOSFET is called off MOSFET.

Ques) Draw the diagram of Half wave Rectifier.

Ques) Draw the diagram of Full wave bridge rectifier.

Ques) What is the value of  $I_{rms}$  in HWR and Full wave rectifier.

Ques) Draw the diagram of Full wave voltage Doubler.

Ques) Why BJT is called a bipolar transistor.

Ques) Write Shockley's Eq<sup>n</sup>.

Ques) What is Modulation?

Ques) What are universal gates?

## 5 MARKS QUESTIONS

Ques) Draw Circuit Diagram of integrator using OP-Amp and Explain its Working. Also Obtain Expression for its Output.

Ques) Draw the circuit of Subtractor using OP-Amp and Explain its working. Also obtain its Expression for its Output.

Ques) Draw Circuit Diagram of differentiator using OP-Amp and Explain its Working. Also Obtain Expression for its Output.

Ques) Explain the following :- With Diagram & working.

i) Full Wave Rectifier

ii) Bridge Rect Half wave Rectifier

Ques) Draw and discuss Voltage tripler Circuit.

Ques) Draw and Explain the Working of a Bridge Rectifier with input and output waveform. Calculate Efficiency and ripple factor.

Ques) Draw and Explain the center-tapped transformer full-wave Rectifier.

A Full wave Rectifier use  $R_L = 2K\Omega$ , Each diodes is to have forward resistance  $R_F = 2\Omega$  and  $R_F = \infty$ . A sinusoidal voltage having each amplified of 20V is applied



Find But,

- i) Peak, dc and rms value of load.
- ii) DC Output power
- iii) AC input
- iv) Efficiency.

Ques) Draw and Discuss Voltage Doubler Circuit.

Ques) Describe the Construction, Working and Characteristics of Enhancement type MOSFETs.

Ques) Explain the Construction and Working of Depletion MOSFET.

Ques) Draw the input and output characteristics of CE NPN transistor configuration with proper label.

Ques) Draw input and output characteristics of a BJT transistor in CE configuration.

Ques) Derive the Relation b/w  $I_{CB0}$  &  $I_{CEO}$ .

## NUMERICALS

Ques) In a Full wave rectifier the load resistance is  $2k\Omega$ ,  $V_f = 400\text{ mV}$ , voltage applied to each diode is  $240\sin\omega t$ . Find

i) Peak value of current ( $I_m$ )


ii) DC value of current ( $I_{dc}$ )

iii) RMS value of current  $I_{rms}$


iv) Efficiency

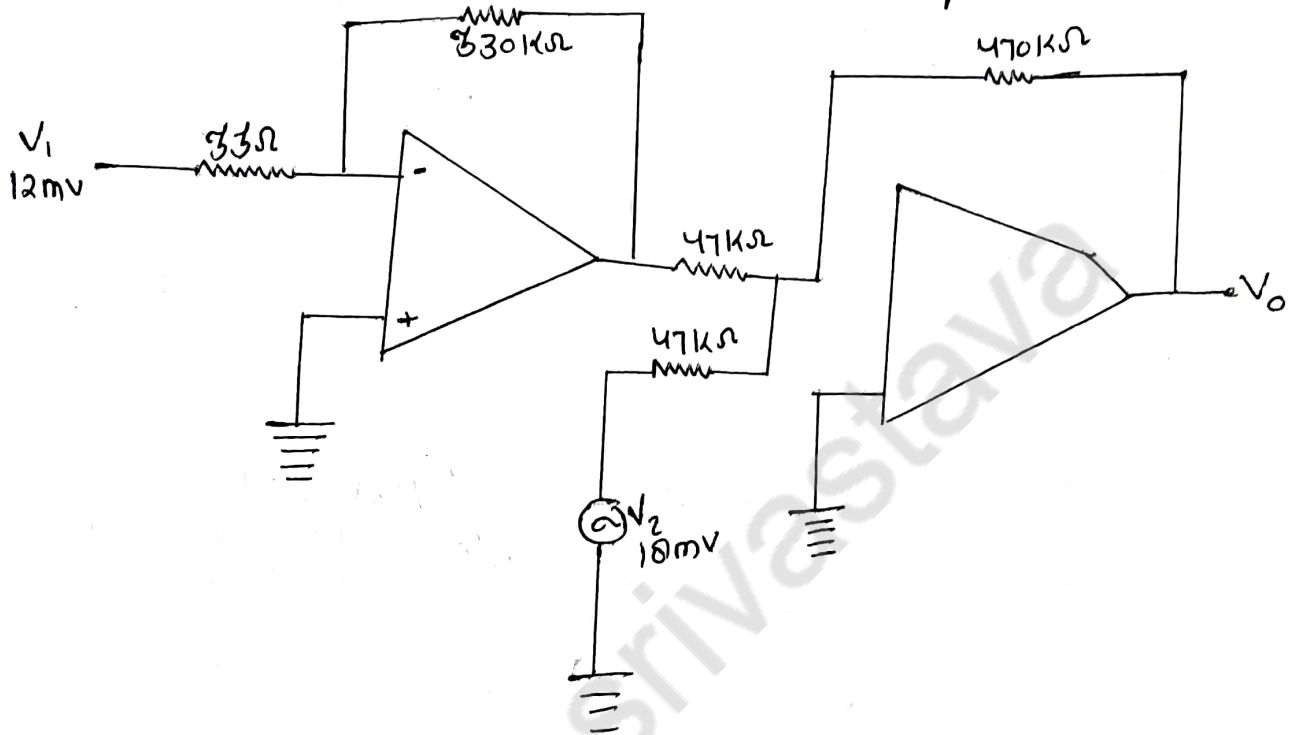v) Ripple factor



Ques) Calculate the Output Voltage  $V_o$  of the circuit.




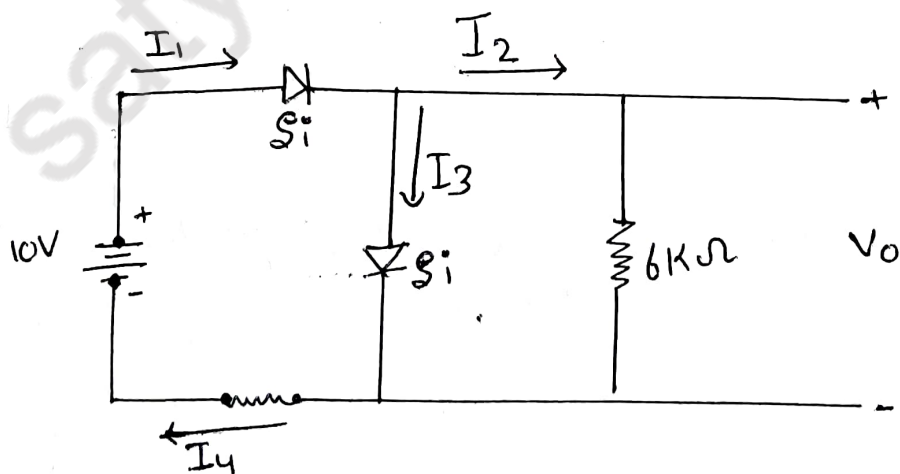
Ques) For the Circuit Shown Figure below determine  $I_1, I_2, I_3, I_4, V_o$ .



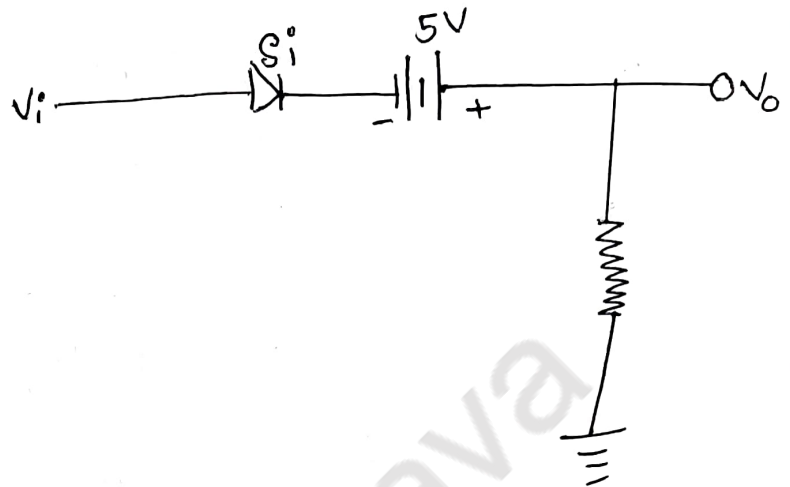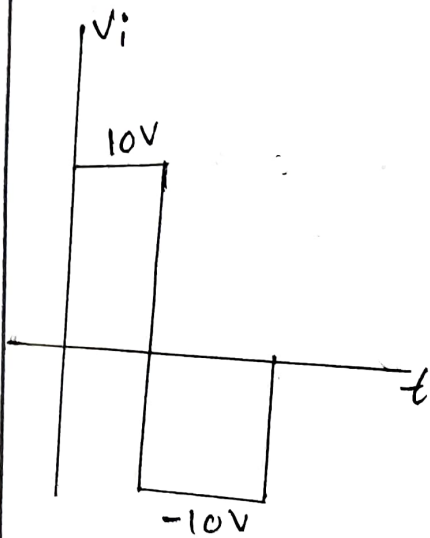
Ques) Determine and sketch  $V_o$  for the given network shown in Fig.



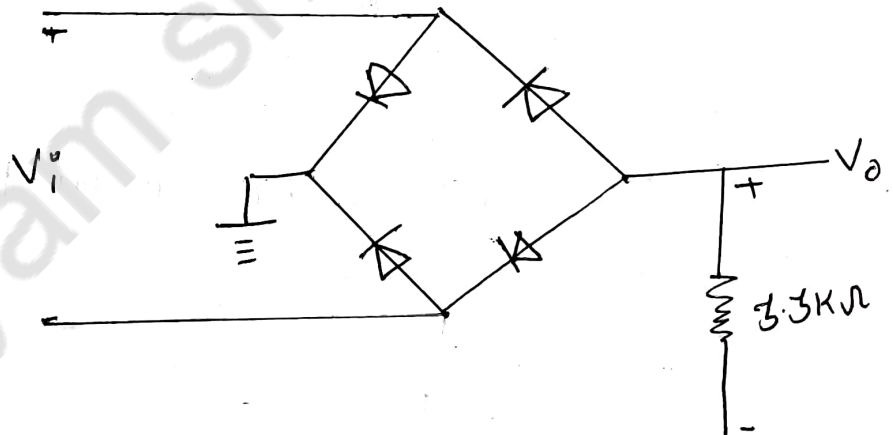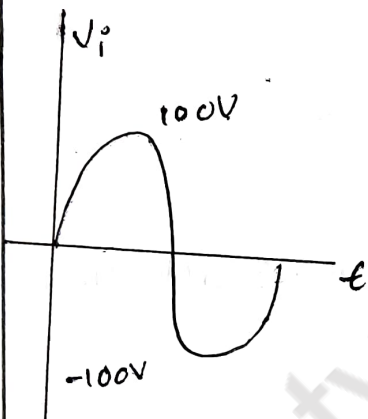Ques) Determine  $V_o$  and the required PIV rating of each diode for the configuration of Fig.



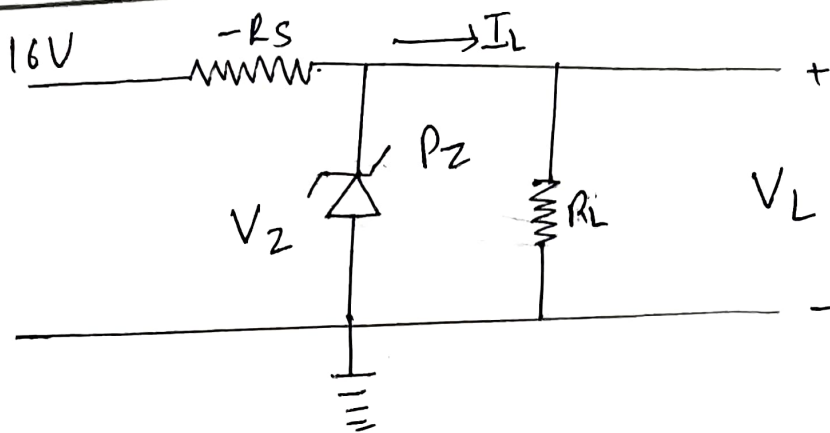Ques) A Sinusoidal signal with peak value 6mA and 2kHz frequency is applied to the input of an Ideal Op-Amp Integrator with  $R_i = 100k\Omega$  and  $C_f = 1\mu F$ . Find Output Voltage.



Ques) Explain the element of a Communication system with the help of block diagram

Ques) A certain AM transmitter radiates 9kW with the carrier unmodulated and 10.125kW when the carrier is Modulate. Calculate the Modulation index.

Ques) i) Minimize the following using K-Map technique  

$$F(A, B, C, D) = \sum m(0, 3, 5, 7, 11, 13) + d(4, 6, 14, 15)$$

ii) Also implement the simplified function using Basic gates.

iii) Also implement the simplified function using NAND Gate only.


iv) Also implement the simplified function using NOR Gate only.

Ques) A Bridge type circuit shown in Fig in the diode are assumed to be ideal. Find.

i) Dc output Voltage


ii) Peak inverse Voltage

Output frequency  
4:1

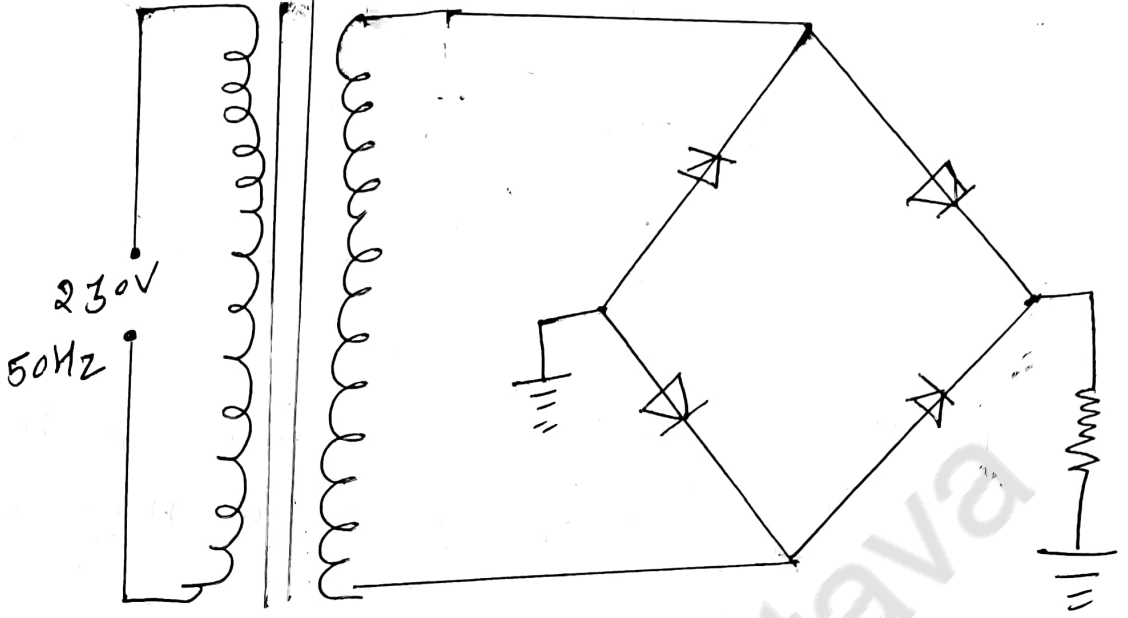




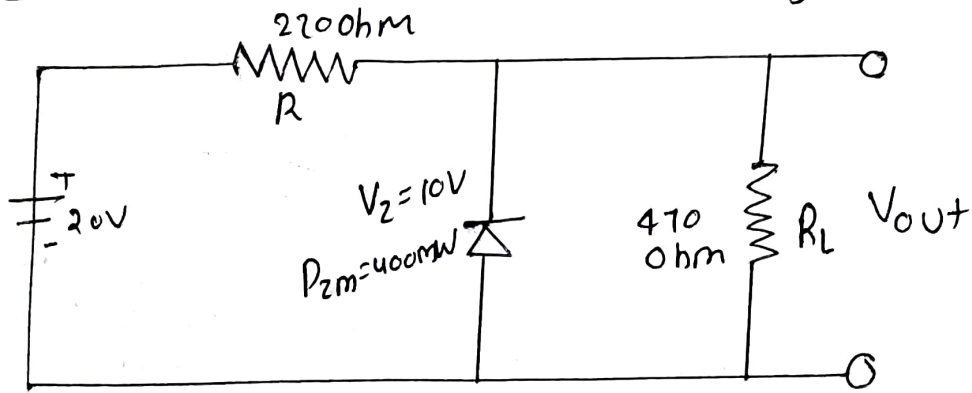
Ques) Determine  $V_L$ ,  $I_L$ , and  $I_Z$  for given Zener diode network as shown in Fig.



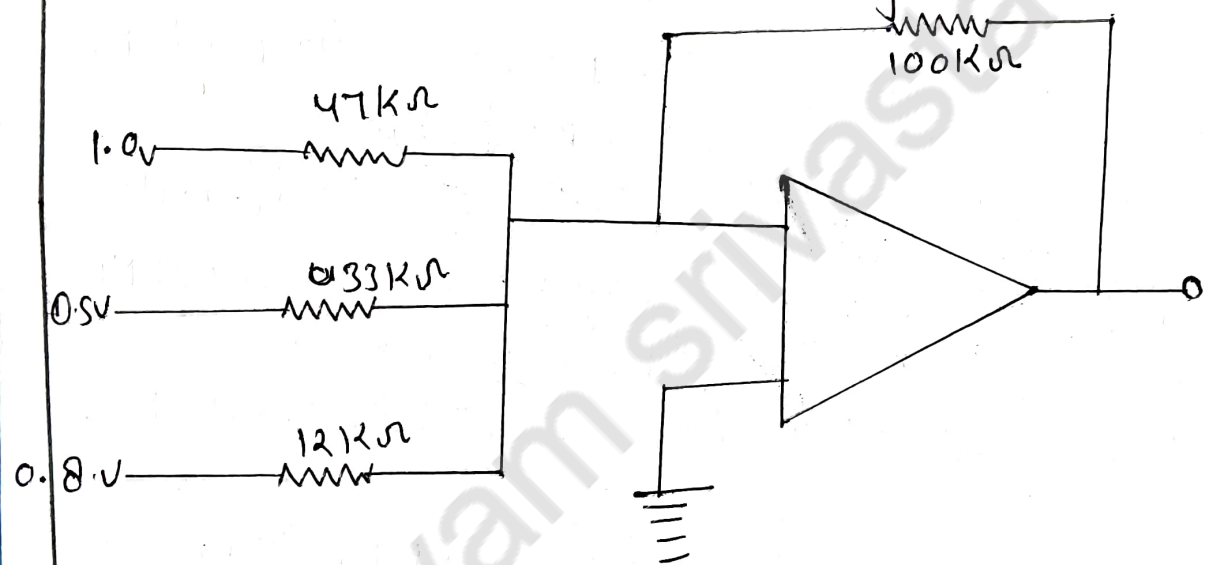
Ques) Determine the Output Voltage of the op-Amp circuit as shown in Fig.



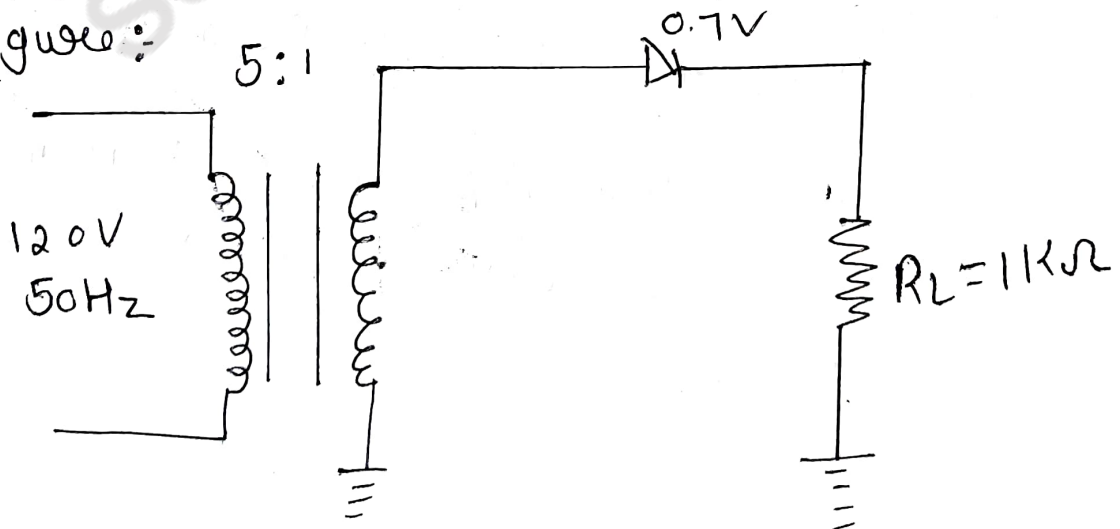Ques) Determine the peak load and DC load voltage for the given rectifier as shown in Figure:



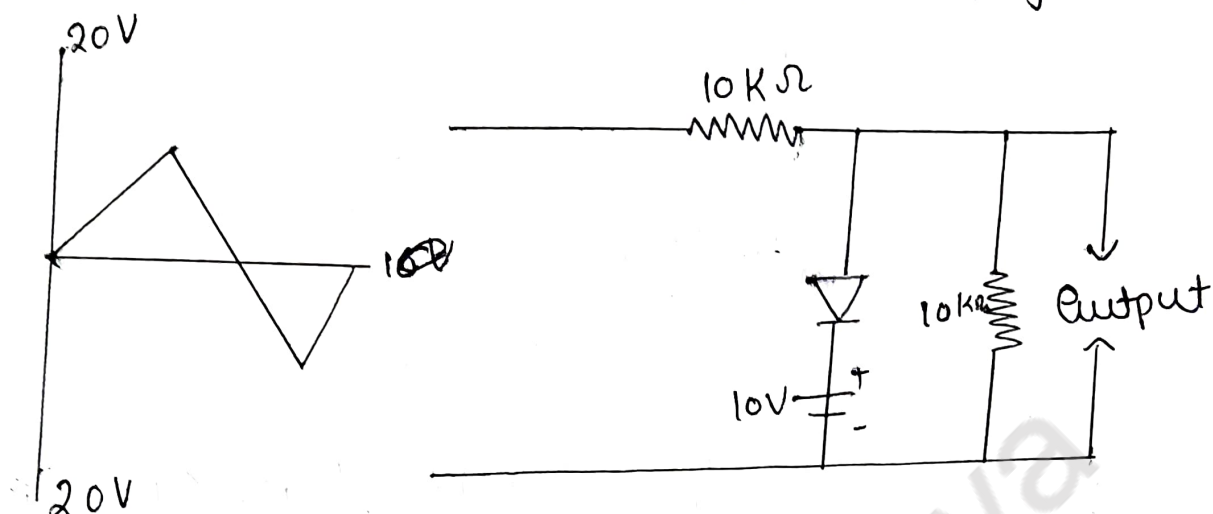Ques) Draw the Output Waveform for the following circuits for the input waveform in Fig.



Ques) Simplify the following Expression using K-MAP in Sum of Products (SOP) form.

$$F(A, B, C, D) = \sum m(1, 3, 4, 6, 8, 9, 11, 13, 15) + \sum d(0, 2, 14)$$

b) Simplify the following Expression using K-MAP in product of SUM (POS) form.

$$F(A, B, C, D) = \prod M(0, 1, 3, 6, 7, 8, 9, 11, 13, 14, 15)$$

Ques) Minimise the following using K-MAP technique.

Also implement simplified function using

NOR Gates :-

$$f(A, B, C, D) = \sum m(1, 2, 9, 11, 15) + \sum d(8, 10, 14)$$

Ques) Calculate the value of  $R_s$  and  $R_L$  to maintain  $V_L$  at  $12V$  for  $I_L$  to vary from  $0$  to  $200mA$ .  
Also find  $V_Z$  and  $P_{Zmax}$ .